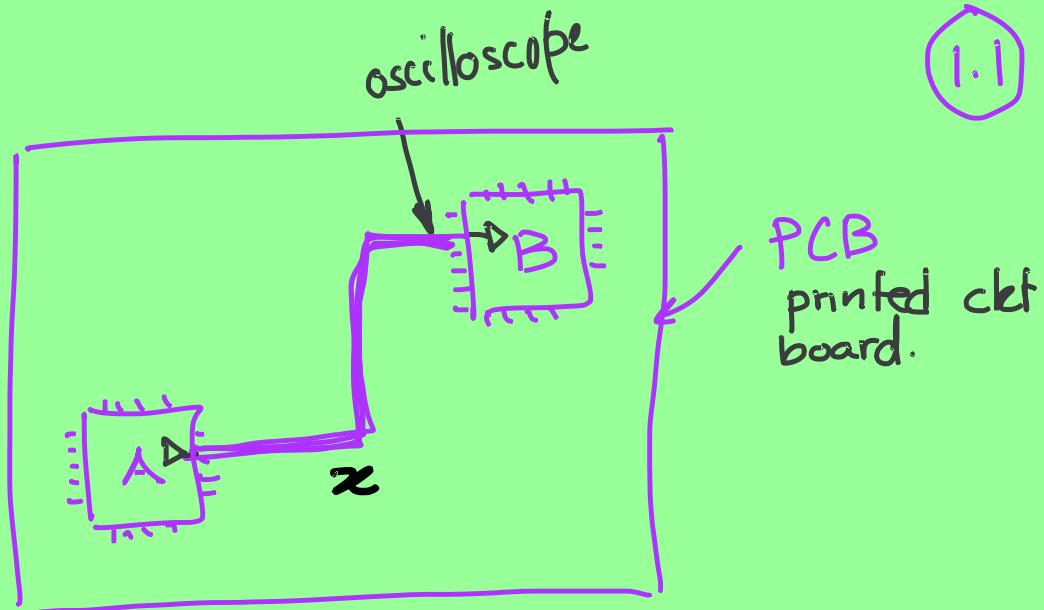


# Transmission Lines


---

- Outline
  - When to Invoke a Transmission Line Model
  - Equations for Propagation
  - Reflections

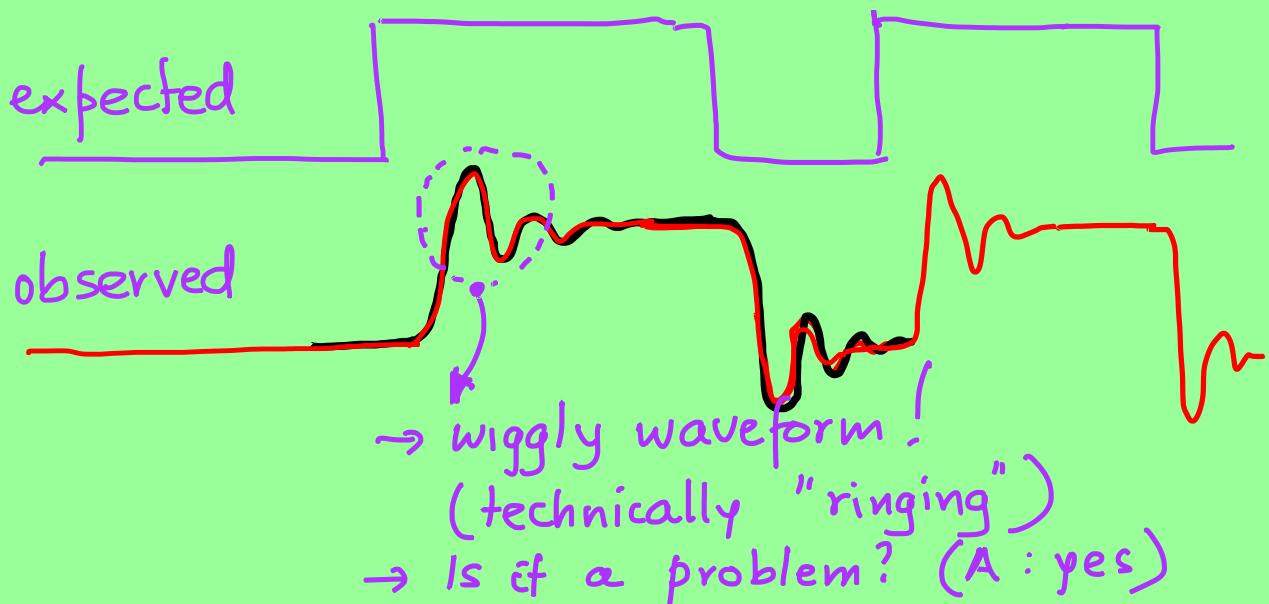1.1




- chip A drives a signal  $\alpha$  to chip B
- I probe signal  $\alpha$  at chip B.



(1.2)

Why is ringing a problem?

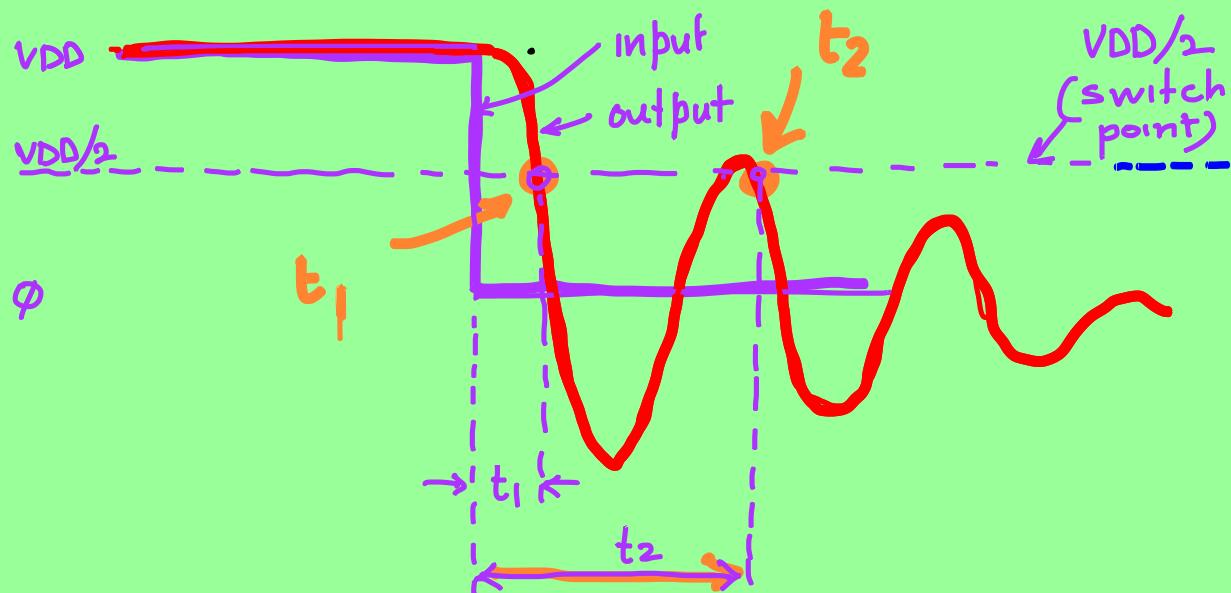


Without ringing  $\rightarrow$  delay is  $t_1$

With ringing  $\rightarrow$  delay is  $t_2 > t_1$  [NOT GOOD!]

How to   
 (a) model ringing in spice?  
 (b) model ringing analytically  
 So we can control it?

① How to model ringing? in Spice

(1.3)

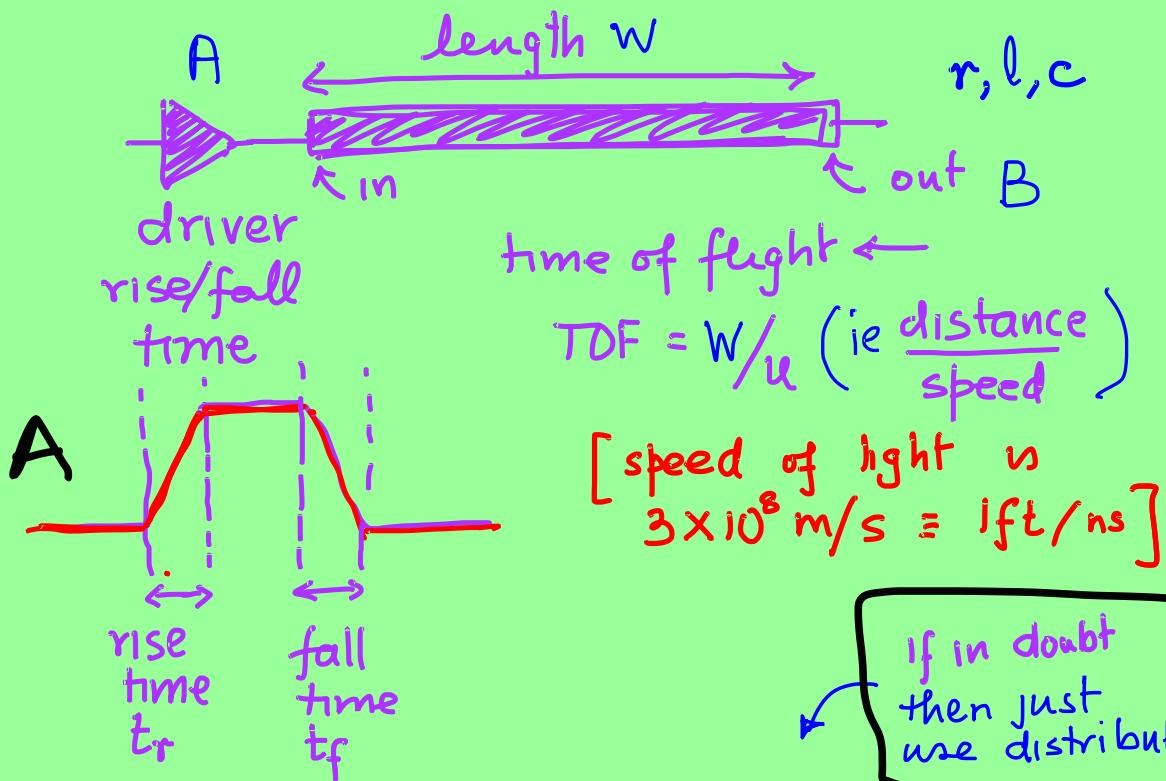

if  $t_r (\approx t_f) \ll TDF$

we need to model ringing  
(wire is treated as a transmission line) "distributed"

else

we don't need to model "lumped"  
ringing. Wire is not treated  
as a transmission line

Lumped (no ringing modeled) ①.4  
(no transmission line)


$l, r, c$  are in a single "lump"



[Delay  $\sim RC$ ] (estimate)

Distributed (transmission line)

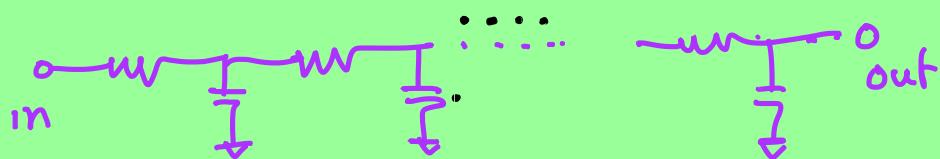$l, r, c$  are "spread out" over the length of the wire [next page: how?]




lots of little resistance/capacitance  
whose total is  $r/c$

[Delay  $\sim RC/2$ ] (estimate)


How to model the wire as a transmission line?

1.5

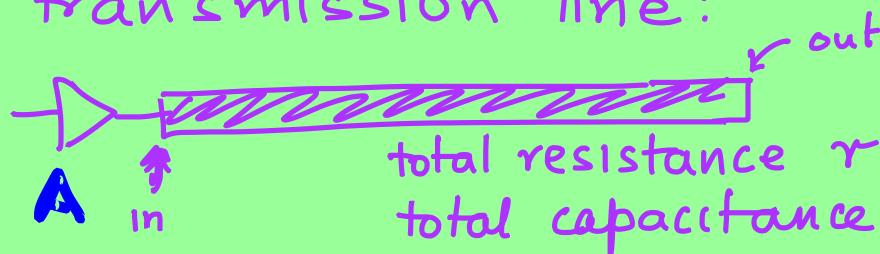

"Distribute" the  $r, c$  into  $T$  or  $\Pi$

sections

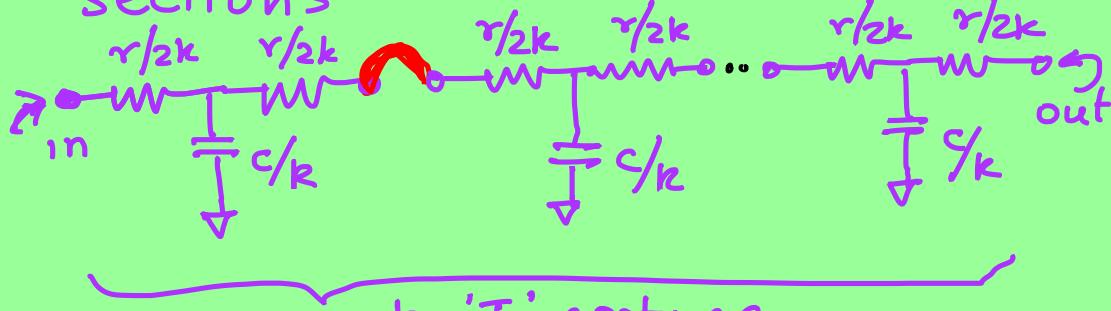

$T$

$k$  'T' sections

$\Pi$

$k$  ' $\Pi$ ' models

Q: Which one  $T$  or  $\Pi$ ?  
A: either!

How many sections? ①.6

→ no universal answer

→ choose  $k$  experimentally

→ Try 1, 2, 3, 4... sections  
and stop at a value

ST the delay difference  
between  $k-1$  and  $k$   
is within an error  
tolerance that you  
want.

# When to Invoke a Transmission Line Model


---

- Suppose we have a wire. When is it to be viewed as a transmission line?
- **Short answer:** When the *time-of-flight* through the wire is comparable or larger than the rise/fall time of the source signal
- Time of flight is known if we know the velocity of wave propagation and the length of the wire. If the velocity of wave propagation is  $u$  and the length of the wire is  $l$ , then
$$u = \frac{l}{t}$$
- What if we need to model a wire as a transmission line?
  - We simply model the R/L/C of the wire in a **distributed** manner instead of a lumped manner.
  - This simply means using several  $\pi$  or  $T$  sections as appropriate (depending on the desired accuracy).
- OK, what about the long answer?
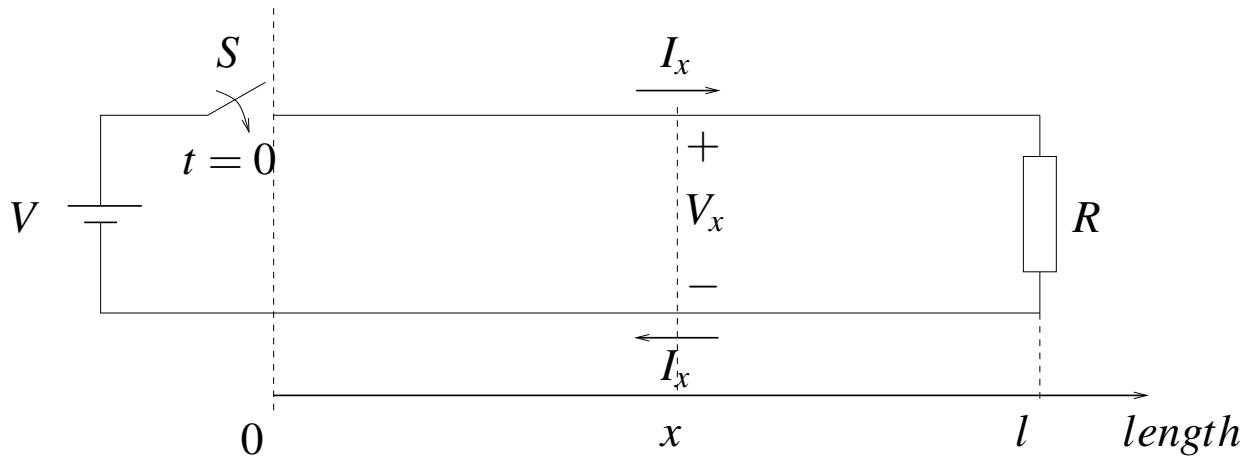
# Equations of Propagation

---





- Consider a wire of length  $l$ , connected to a voltage source  $V$ , and a switch  $S$  as shown below. The load resistance  $R$  is connected at the end of the wire.
- At time  $t = 0$ , the switch  $S$  is closed.



- The effect of closing  $S$  is not felt everywhere immediately
- Rather, this effect propagates from the source to load with a **finite** velocity
- Assuming uniform cross section, this velocity is given by  $u = \frac{1}{\sqrt{LC}}$ . Here  $u = \frac{c}{\sqrt{\kappa}}$ , where  $\kappa$  is the dielectric constant of the medium in which the wire resides.  $L$

and  $C$  are the inductance and capacitance per unit length of wire.

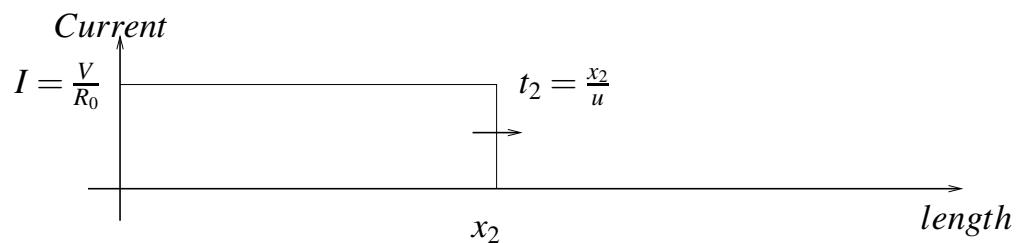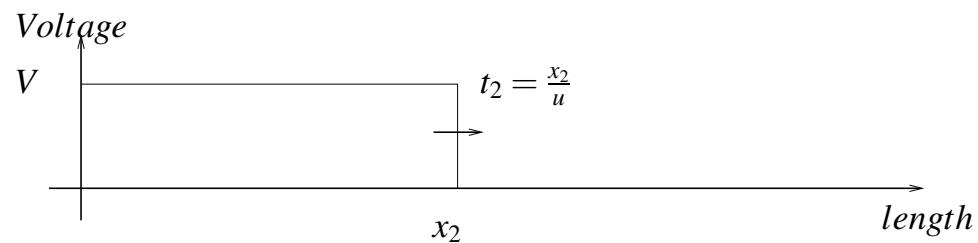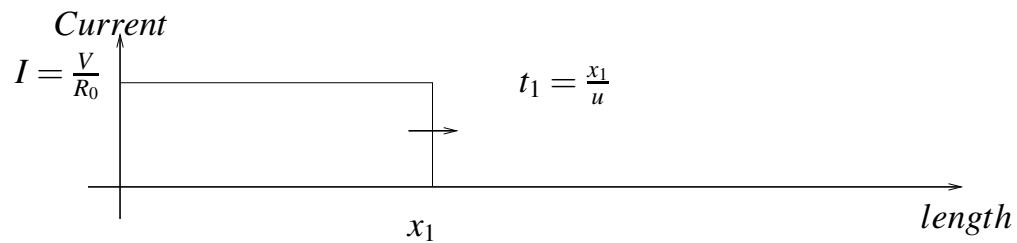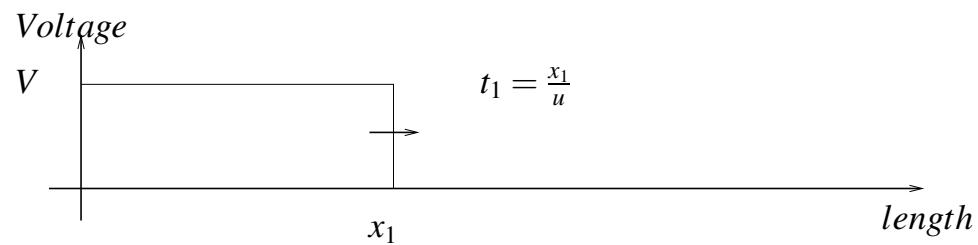
- Note that if  $L$  increases,  $C$  decreases and vice versa.
- The voltage/current distributions on the wire at times  $t_1 = x_1/u$  and  $t_2 = x_2/u$  are shown below.



- We introduced a quantity  $R_0$  above. How is it computed and what is it? Lets explain this analytically
- At  $t_1$ , the voltage is  $V$  for  $0 \leq x \leq x_1$  and 0 for  $x_1 < x \leq l$
- In other words, a **front** of voltage travels to the right with velocity  $u$ .
- Lets say this front moves a distance  $dx$ . Then the capacitance to be charged is  $Cdx$  (since  $C$  is the capacitance per unit length)
- The charge required is  $dQ = VCdx$ . Hence the current is given by
- $I = \frac{dQ}{dt} = VC \frac{dx}{dt} = VCu = VC \frac{1}{\sqrt{LC}} = V \sqrt{\frac{C}{L}} = \frac{V}{R_0}$
- $R_0 = \sqrt{\frac{L}{C}}$  the **Characteristic Impedance** of the line.
- It is a function of the medium in which the wire resides. For PCBs,  $R_0$  is in the 50-75  $\Omega$  range.
- The expression for  $I$  above is the current for  $x=0$  to wherever the front is. To the right of the front,  $I=0$ .

- We say that  $I_x$  is positive when current flows to the right in the top wire, and to the left in the bottom wire.
- For all  $x$  from 0 to the location of the front (call it  $x$ ), we have  $V_x/I_x = R_0$ .
- If the source and load were interchanged, we would have  $V_x/I_x = -R_0$  based on our sign convention

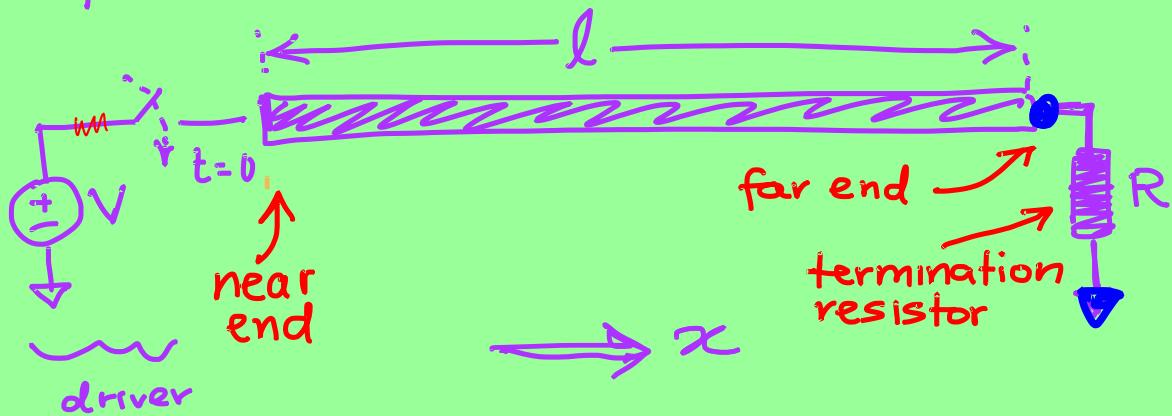b) Analytical model for transmission line:



$$\frac{\text{inductance}}{\text{length}} = L$$

$$\frac{\text{capacitance}}{\text{length}} = C$$

lowercase  
c, speed  
of light.  
 $c = 3 \times 10^8 \text{ m/s}$

$$u = \frac{c}{\sqrt{L/C}} = \frac{1}{\sqrt{LC}} = \text{speed of wave}$$

dielectric  
constant


[approx. 1 foot/ns]

$K \sim 4$  for most  
PCB

PCB material is  
called FR4

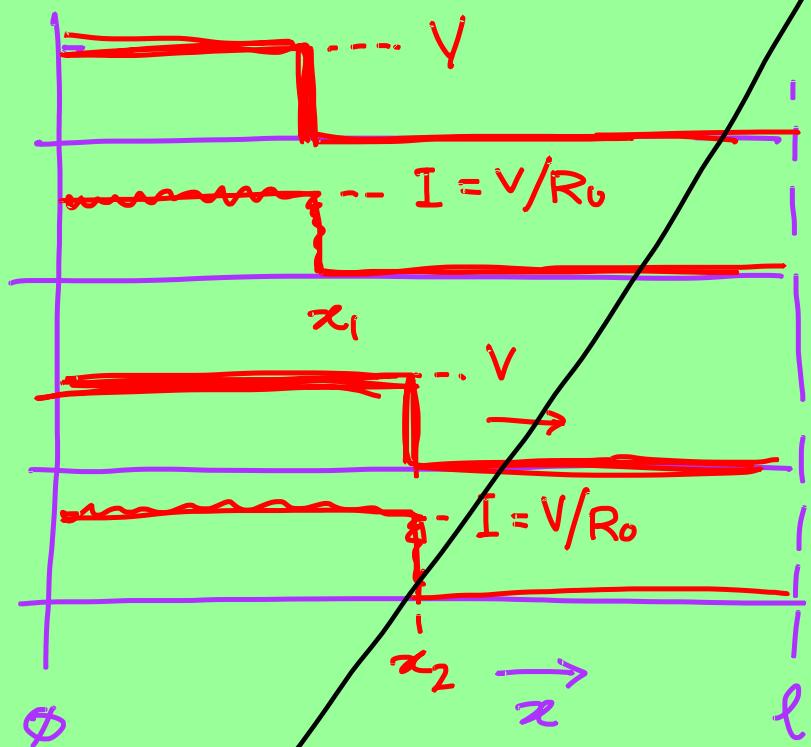(3.2)

- A wave of voltage (and current) moves from left to right




$$@ t_1 = \frac{x_1}{u}$$

say  $t_2 > t_1$ :

$$@ t_2 = \frac{x_2}{u},$$

$$t_2 > t_1$$

$\frac{V}{I} = R_0$  is a key (and non-intuitive)  
quantity!  
= characteristic impedance of wire  
=  $Z_0$

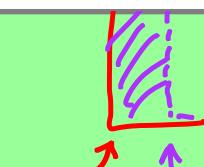Finding  $R_0$ 

(3.3)

(ie move  $dx$ , in time  $dt$ )

→ Suppose wave has reached location  $x$  at time  $t$

→ In time  $\underline{dt}$ , it travels an extra distance  $dx$

$$\frac{dx}{dt} = U = \frac{c}{\sqrt{K}} = \frac{1}{\sqrt{LC}}$$

from 3.1

→ In distance  $dx$ , the additional capacitance charged is  $C \cdot dx$

→ Recall that  $(Q = C \cdot V)$

charge = capacitance  $\times$  voltage

→ So the <sup>electrical</sup> charge needed to charge the additional capacitance  $C \cdot dx$  from  $\emptyset$  to  $V$  volts is

$$\text{d}Q = (C \cdot dx) \cdot V$$

→ This is done in time  $dt$ . So

$$\frac{dQ}{dt} = C \cdot V \cdot \frac{dx}{dt}$$

$$I = C \cdot V \cdot u$$

$$\frac{I}{V} = C \cdot u = C \cdot \frac{1}{\sqrt{LC}} = \frac{I}{R_0}$$

$R_0 = \sqrt{\frac{L}{C}}$  (called characteristic impedance)

not a physical resistor


$$R_0 = 50-75 \Omega$$

3.4

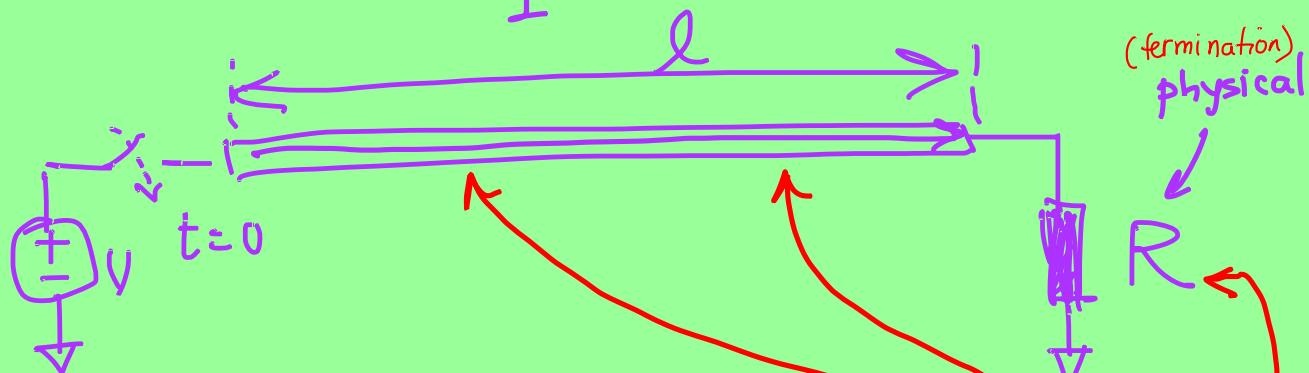3.5

$R_o$  is NOT a physical resistance!! It just "springs into life" when there is a wave of  $V$  &  $I$  traveling in the wire, and it relates the  $V$  wave magnitude to the  $I$  wave magnitude

$$R_o = \frac{V}{I} \text{ for a moving wave}$$



So when the wave is moving in the wire,  $\frac{V}{I} = R_o$

But when the wave reaches the far end, we need  $\frac{V}{I} = R$

WHAT IF  $R \neq R_o$ ???

## Reflections

---

- If the length  $l$  was infinite, then the front would keep moving to the right.
- If  $l$  is finite, then but if the load resistor  $R = R_0$ , then when the front arrives at the load (at time  $l/u$ ), currents at all points in the wire and the load are  $V/R_0$ , and so nothing further happens.
- It is as though the length  $l$  was infinite.
- Now lets suppose  $R \neq R_0$ . When the front arrives at the load (at time  $l/u$ ), the current in the wire is  $V_x/R_x = R_0$ . But **at the load**, the relationship  $V_l/R_l = R$  **is required**.
- This causes a discontinuity. Thus a **reflection** develops at the load, which moves to the left.
- The amplitude and polarity of this reflected wave are such that the **total** voltage  $V_l$  (i.e. sum of the incident and reflected voltage) is related to  $I_l$  by the expression  $V_l/I_l = R$
- If the incident voltage was  $V$ , the reflected voltage will be  $\rho V$  where  **$\rho$  is the reflection coefficient**

- If the incident current is  $V/R_0$ , reflected current is  $-\rho V/R_0$  based on our sign convention.
- The ratio of the total voltage to total current is  $R$ , therefore  

$$R = \frac{V+\rho V}{V/R_0-\rho V/R_0}.$$
- Solving, we get  $\rho = \frac{R/R_0 - 1}{R/R_0 + 1}$ . This reflection coefficient ranges from  $-1$  to  $+1$ .
  - When  $R = R_0$ , then  $\rho = 0$ . So no reflections are observed (we agreed that should be the case above).
  - When  $R = \infty$  (i.e. the wire is **unterminated**),  $\rho = 1$
  - When  $R = 0$  (i.e. the wire is short-circuited),  $\rho = -1$
- There can be several reflections in this manner. We can compute the waveform at  $l$  by accounting for such reflections.

when the wave reaches the far end.... 2 cases

4.1

(1)  $R = R_0$

$$\frac{V}{I} \text{ along the wire} = R_0$$

$$\frac{V}{I} \text{ when wave reaches end} = R \\ (= R_0)$$

So it's like the wave kept on traveling... crisis averted!

(2)  $R \neq R_0$

$$\frac{V}{I} \text{ along the wire} = R_0$$

$$\frac{V}{I} \text{ when wave reaches end} : R \neq R_0 \\ \underline{\text{CRISIS!!}}$$

→ Solution launch a reflected wave back towards the near end.

→ its voltage is  $\ell \cdot V$  } so  $\frac{\ell V}{R I} = R_0$  as

→ its current is  $\ell I$  }  $R I$  reqd.  
(but its sign is -ve)

So, at far end : physical (terminating res.)

$$\frac{\text{total voltage}}{\text{total current}} = R = \frac{V + \ell V}{I - \ell I}$$

Massage the math:

(4.2)

$$\rho = \frac{R/R_0 - 1}{R/R_0 + 1}; \quad \rho \equiv \text{reflection coefficient}$$

NOTES •  $-1 \leq \rho \leq 1$

•  $R = R_0 \Rightarrow \rho = 0$

•  $R = \infty \Rightarrow \rho = 1$  (open ckt-termination)

•  $R = \emptyset \Rightarrow \rho = -1$  (short ckt-termination)


Reflected wave  
if  $\rho \cdot V = \emptyset \cdot V = \emptyset$ .  
(no reflection)  
(matches intuition  
of 4.1)

Reflected wave  $\rightarrow$   
 $\rho V = -V$ , so total  
voltage @ far end is  
 $V + \rho V = V - V = \emptyset$   
(matches intuition)

Reflected wave  $\rightarrow \rho V = 1 \cdot V = V$ .  
So total voltage @ far end is  
 $V + V = 2V$ . OUCH. Can damage  
far end chip input circuitry!


# Workspace for 'transmission-lines'

Page 16 (row 3, column 9)

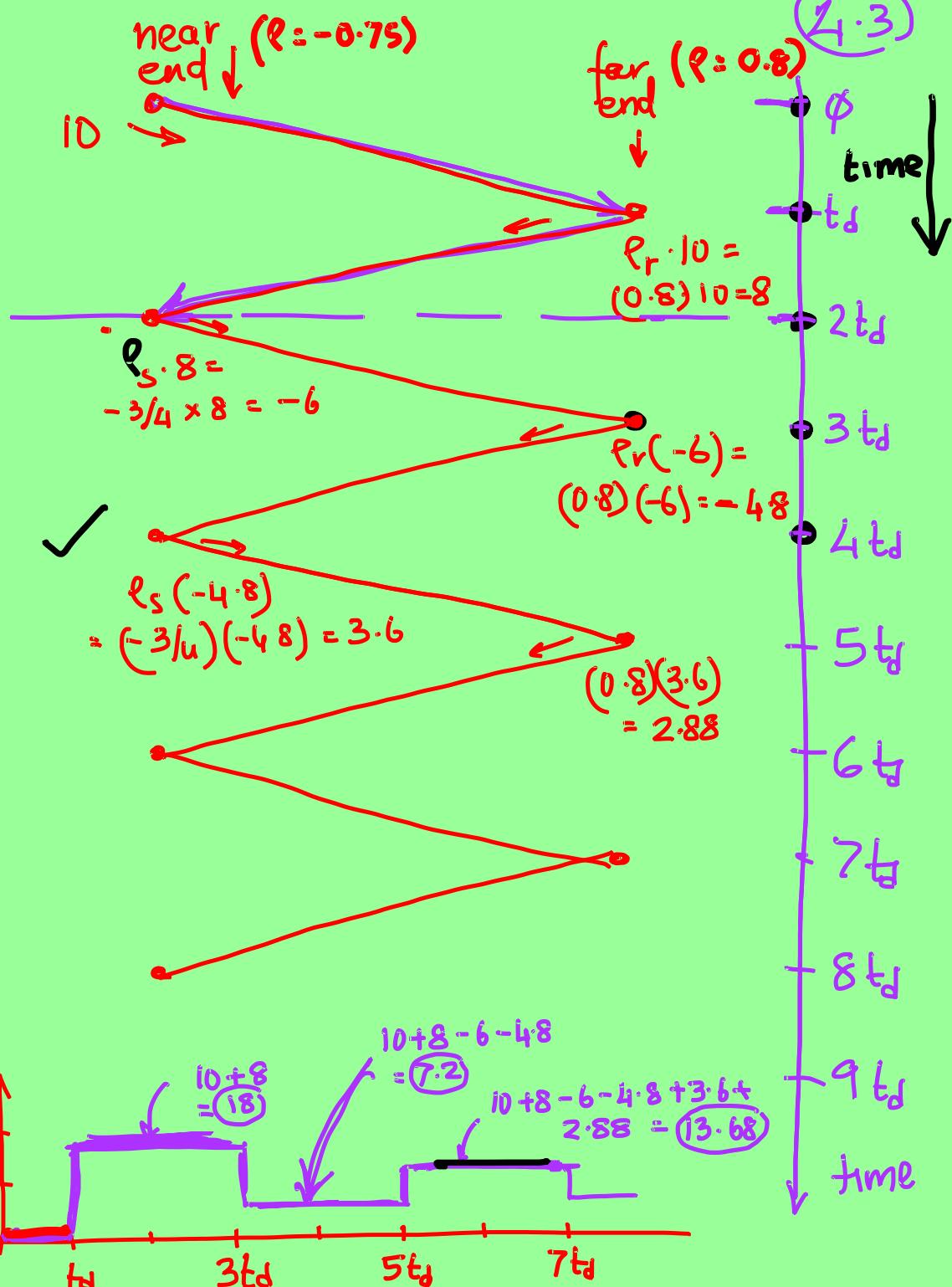

(4.4)

Far end voltage looks like

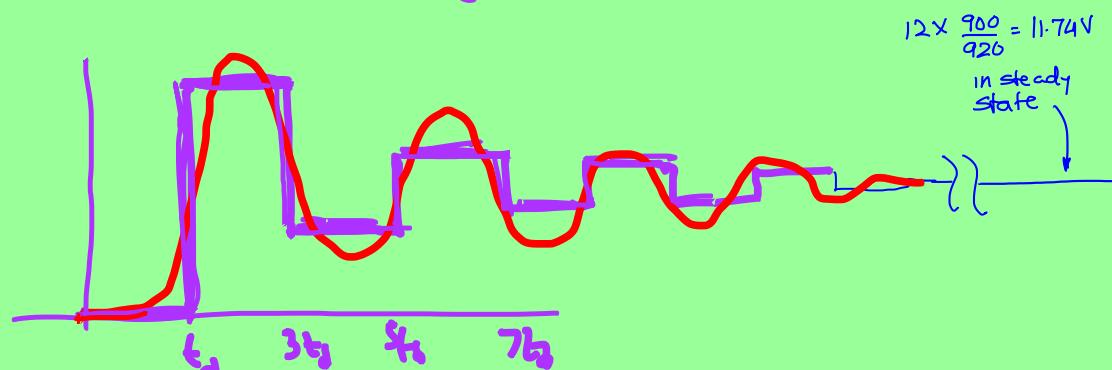

⊗ Just like the red waveform in 1.1 and 1.2 !!

⊗ if we want the voltage to never exceed  $X$  volts @ far end, just make sure that

$$V + \rho V = X$$

[ If  $R_o = 50\Omega$ ,  $V = 2.5V$  and  $X = 3V$ , then ]

$$2.5 + \rho(2.5) = 3$$

$$\rho = 0.2 = \frac{R/R_o - 1}{R/R_o + 1}$$

calc.  $R$ ]

(4.5)

⊗ frequency of ringing  $\nu$ 

$$\left(\frac{1}{4L_d}\right) = \frac{1}{4(l/u)}$$

 $l$  is wire length $u$  is speed of wave (see 3.1)

4.6

For no reflections }  
(ie no ringing) }       $R = R_o$

Problems w/  $R = R_o$

→ every PCB trace/wire needs  
a resistor

→ expensive (\$)

→ expensive (pwr)

→ expensive (board area)


→  $R_o \sim 50\Omega$

$R = 50\Omega$  also


$$i = \frac{V}{R} = \frac{V_{DD}}{50} = \frac{2.5V}{50}$$

$\boxed{50mA}$
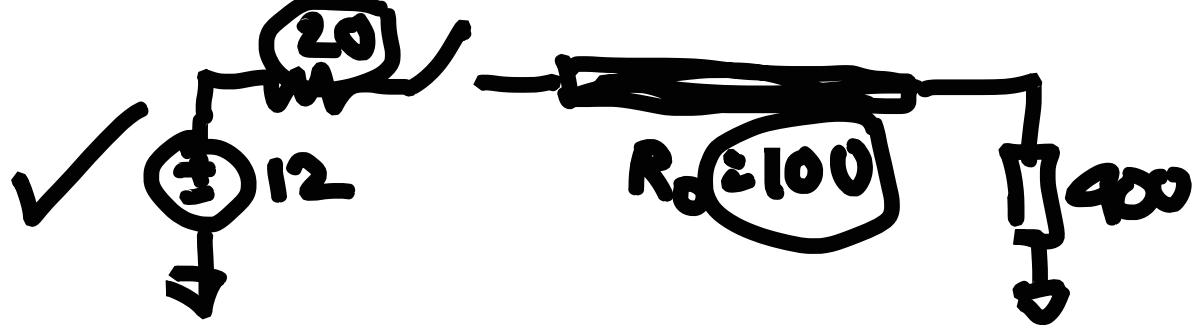
$$\left( \frac{50}{1000} \times 10000 \right) = 500A$$



## Reflections - An Example


---

- Consider a wire of length  $l$ , with  $R_0 = 100\Omega$ ,  $R = 900\Omega$  and a source resistance  $R_s = 20\Omega$ . Also assume the source voltage is  $V = 12V$ . We want to determine the waveform at the end of the wire
- First we compute the reflection coefficients.
  - $\rho_R = \frac{\frac{900}{100} - 1}{\frac{900}{100} + 1} = 0.8$  (A)
  - $\rho_S = \frac{\frac{20}{100} - 1}{\frac{20}{100} + 1} = -0.75$  (B)
- A 12 V step appears on the line as a step of voltage  $V_1 = 12 \frac{R_0}{R_0 + R_s} = 10V$
- At time  $t = t_d = \frac{l}{u}$ , the wave  $V_1$  arrives at the end of the line, where it is reflected as:  

$$V_2 = \rho_R \cdot V_1 = 0.8 \cdot 10V = 8V$$
- Therefore the receiver voltage at this time is  $V_1 + V_2 = 18V$
- At time  $2 \cdot t_d$ , the wave  $V_2$  arrives at the source. It is now reflected as:  

$$V_3 = \rho_S \cdot V_2 = -0.75 \cdot 8V = -6V$$

- At time  $3 \cdot t_d$ , the wave  $V_3$  arrives at the end of the line. It is now reflected as:  
 $V_4 = \rho_R \cdot V_3 = 0.8 \cdot (-6)V = -4.8V$ .
- So the receiver voltage at this time is  $V_1 + V_2 + V_3 + V_4 = 7.2V$
- And so on...
- Asymptotically, the voltage at the end of the wire is  $V \cdot \frac{R}{R+R_s} = 12 \cdot \frac{900}{920} = 11.739V$  The waveform at the end of the wire therefore looks like:

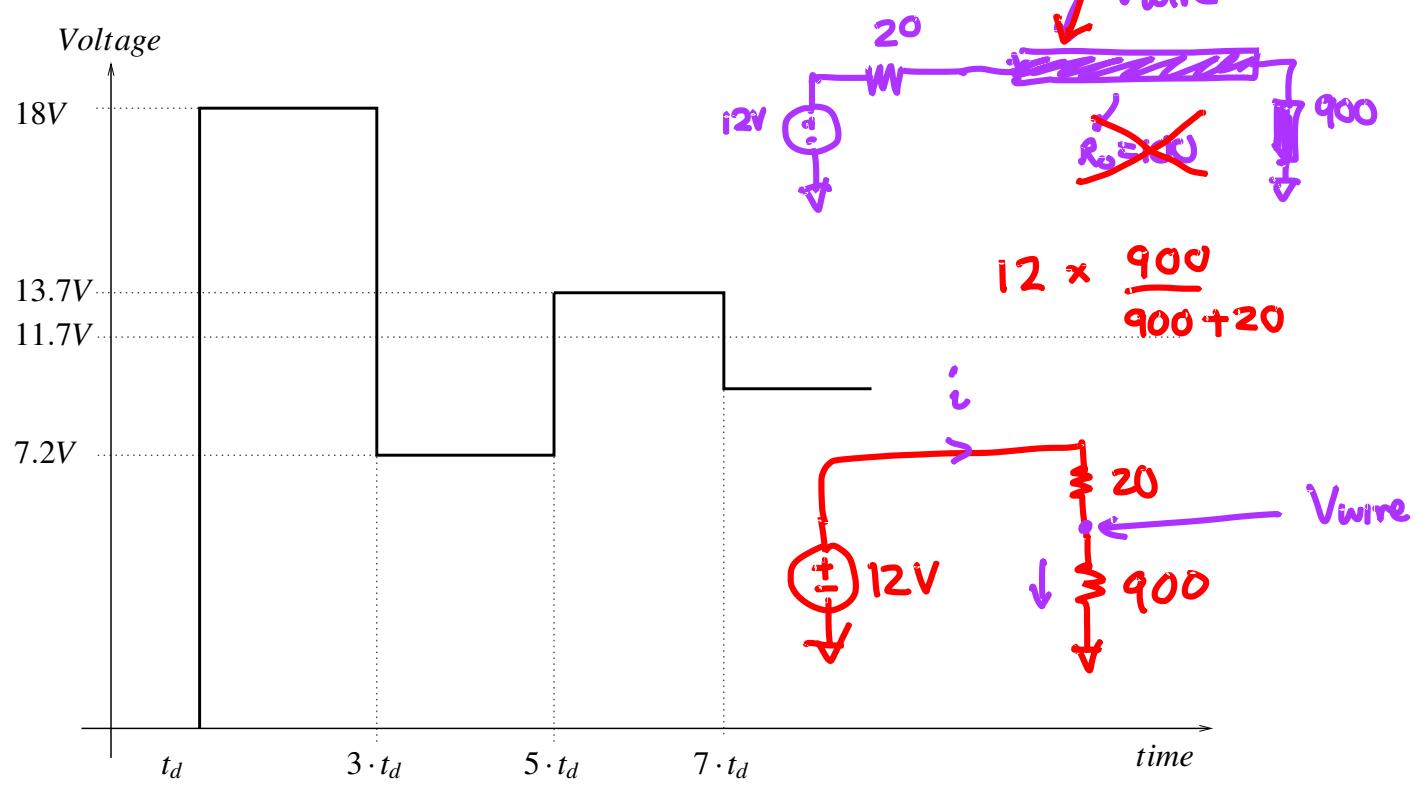

$$I = \frac{V}{R} = \frac{12}{920}$$

$$V_{wire} = I \cdot 900 = \frac{(12)}{920} \cdot 900$$